

Electric Machine – 1

Assignment – 4

By Ansh sharma

24BEE005

Ansh Sharma
24BEE005

17 Explain Sumpner's Back to Back test on Single phase transformer. What are the necessary Condition for this test?

The Sumpner's Back to Back test, also known Regenerative test, is used for finding efficiency and regulation of a Transformer under full-load conditions, without actually loading it.

It is done on two identical single-phase transformers.

* Purpose of the Sumpner's test, →

- 17 To measure the efficiency of a transformer at
- 17 To measure full load losses ($I_{20}R_{20} + G_{20}V_{20}$) loss.
- 27 To Simulate full-load condition (including temperature rise) without connecting an Actual load.
- 37 To reduce power consumption during testing - power drawn is only enough to supply the losses.

* Test Setup, →

Take Two Identical single-phase transformer are required.

- Primaries of both transformer are connected in parallel and supplied from the rated Voltage source.
- Secondaries are connected in opposition (Series adding) so their Voltages opposes each other.

- An auxiliary Voltage Source (low Voltage) is Connected in the Secondary loop to Circulate full-load Current through both transformers.

• Working principle ~

- The Supply to primaries provide the Core (iron) losses, since rated Voltage is applied.
- The auxiliary Voltage in the Secondary causes Circulating full-load Current, which leads to Copper losses in the windings.
- No actual Output load is Connected - yet both transformer experience full-load Conditions.

Necessary Condition for Sumpner's Test, →

1) Two identical Transformers: →

- Same rating (KVA), Voltage ratio, impedance.
- Ensures balanced loading and Symmetrical operation.

2) Rated Voltage on Primaries: →

- Applied from the main supply to determine loss iron correctly.

3) Secondary Connected in opposing polarity.

- When Connected, they should ideally Cancel each other out (zero net Voltage), so a small external Voltage Source can Circulate rated Current.

Ans h sharma
24BEE005

Ash sharma
23BEE005

4. Auxiliary Voltage Source :-

- Needed to Circulate full-load current in secondary loop.
- Should be adjustable and Capable of Supplying rated St Secondary Current.

5. Proper Instrument :-

- Wattmeter on the
→ Primary side: for Core (iron) loss.
→ Secondary Circulating Circuit: For Copper loss


* Advantage:

- Full-load test without actual load.
- Very economical (low power wasted).
- Accurate efficiency & Regulation.
- Checks temperature rise under rated load
- Suitable for large transformers.

Arsh Sharma
21BEE005

- W_1 (Wattmeter) = Connected in Primary Circuit.
→ measure iron core loss.
- W_2 (Wattmeter) = Connected in Secondary Circuit.
→ measure Copper losses.

Diagram

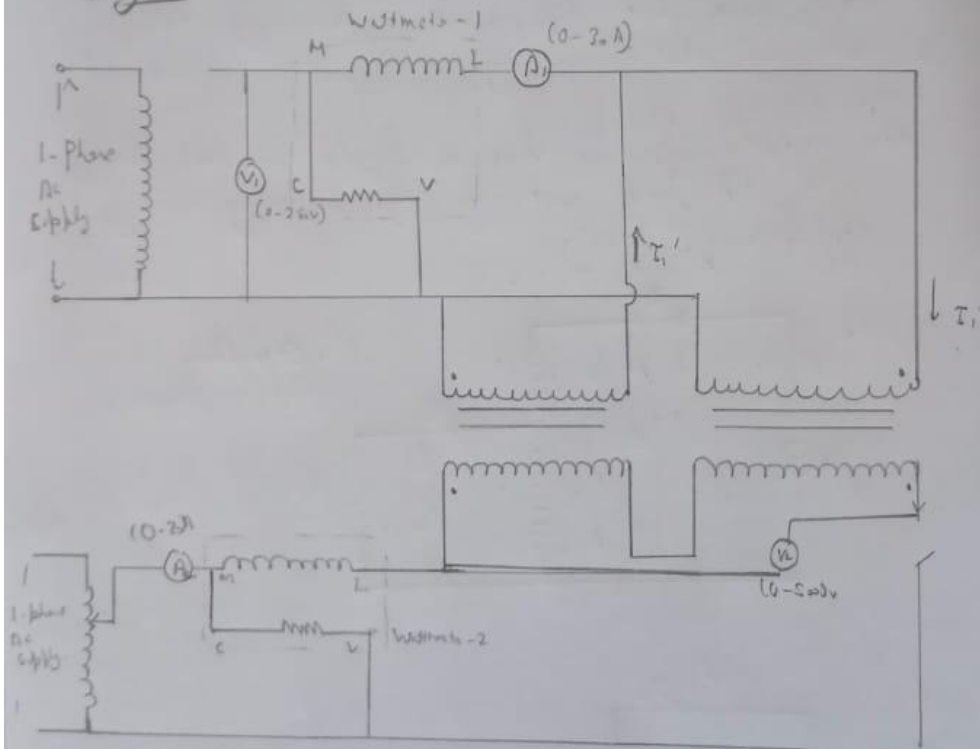


Q7] What is an Auto Transformer?

Derive the equation for Conductive and inductive power transfer in Auto Transformer.


⇒ An auto transformer is a transformer with only one winding on a laminated core.

An auto transformer is similar to two winding transformer but different in the way the primary and Secondary winding are interconnected.

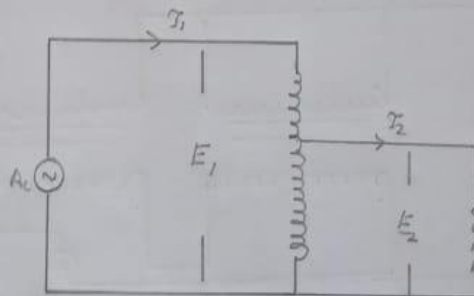An autotransformer has a single consistent winding with tap point between the primary winding and Secondary winding



Step Down
Autotransformer

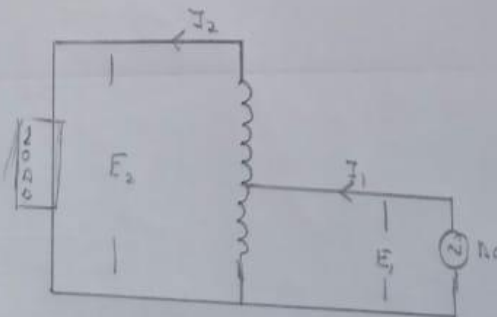

Step up
Autotransformer

For Stepup Auto transformer

Ash Sharma
25BET5005

$$\bullet S(\text{Apparent power}) = V_1 I_1 = V_2 I_2$$

$$\text{Now, } V_1 < V_2 \text{ \& } I_1 > I_2$$

$$\text{At Node B Applying KCL, } I_2 + I = I_1$$

$$\underline{I = I_1 - I_2}$$

• BC : Common Winding

AC : Series Winding

for inductive power transformer, we have chosen Common winding BC.

$$\bullet S_{sd} = V_1 (I_1 - I_2) = V_1 (I_1 - I_1/k) = V_1 I_1 (1 - 1/k)$$

$$\therefore S_{sd} = S (1 - 1/k)$$

$$\underline{S_{total} = S_{sd} + S_{scd}}$$

$$\bullet S = S (1 - 1/k) + S_{scd}$$

$$S_{scd} = S - S (1 - 1/k)$$

$$\underline{S_{scd} = S/k}$$

• For Step Down Auto transformer.

• In IDEAL Transformer.

→ Power Conservation.

$$S(\text{Apparent power}) = V_1 I_1 = V_2 I_2$$

Now, $V_1 > V_2$ $I_1 < I_2$

At node B applying KCL

BC → Common winding

AB → Series winding.

$$I = I_1 + I_2$$

$$I = I_2 - I_1$$

For inductive power transformer we have chosen
Common winding BC.

$$S_{\text{inductive}} = V_2 (I_2 - I_1)$$

$$= KV (I_2 - I_1)$$

$$= V_1 (KI_2 - KI_1)$$

$$= V_1 (I_2 - KI_1) = V_1 (1-K)$$

$$S_{\text{inductive}} = S(1-K)$$

$$S_{\text{Total}} = S_{\text{ind}} + S_{\text{out}} \Rightarrow S(1-K) + S_{\text{out}}$$

$$S_{\text{out}} = S - S(1-K)$$

$$S_{\text{out}} = SK$$